

This problem refers to Example 3 in the “AC-the hard way” lecture notes.

Work through the mathematical details needed to obtain the expressions for the inductor current given in the notes. Be thorough — include all of the steps needed to completely solve the differential equation.