

Find the voltage v_{o1} and v_{o2} in the circuit at right.

Recall: For an op amp with a negative feedback loop,

$v_+ = v_-$.

$v_{o1} =$ _____

$v_{o2} =$ _____

