

Use the mesh-current method to find the currents in R_1 , R_3 , and R_5 in the circuit shown at right.

$i_{R1} =$ _____

$i_{R3} =$ _____

$i_{R5} =$ _____

