

Use the method of superposition to find the values of v_{R2} and v_{R6} in the circuit at right.

$v_{R2} =$ _____

$v_{R6} =$ _____

