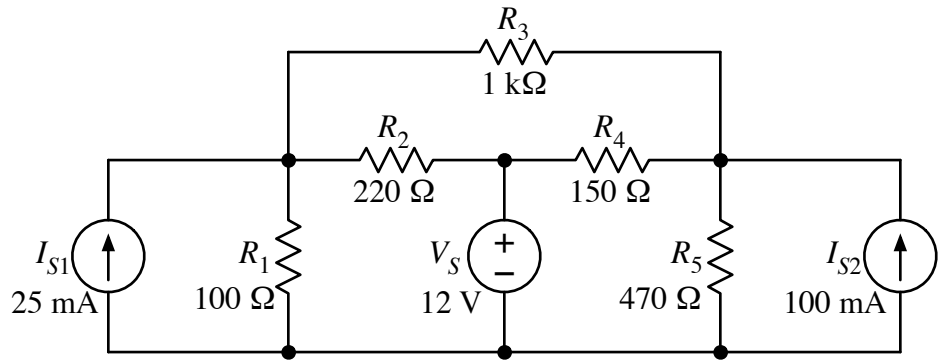


Using the node-voltage method, calculate the power delivered (or absorbed) in each source in the circuit.



$P_{V_S} =$ _____ (delivered / absorbed)

$P_{I_{S1}} =$ _____ (delivered / absorbed)

$P_{I_{S2}} =$ _____ (delivered / absorbed)