

Using the mesh-current method, calculate the power dissipated in each resistor.

$P_{R1} =$ _____

$P_{R2} =$ _____

$P_{R3} =$ _____

$P_{R4} =$ _____

