

For the circuit shown below, use the *source transformation* method to find the voltage v_{R3} . Your procedure will require some “sidesteps” as you work to combine sources and resistors. It is probably a good idea to include sketches of intermediate circuits as you transform your way to a final circuit.

$v_{R3} =$ _____

