

A switching voltage source is connected directly across a 100-nF capacitor. The source voltage increases parabolically from 0 to 5V in 1-ms according to the relation,  $V_S(t) = at^2$  where  $a = 5 \times 10^6 \text{ V} \cdot \text{s}^{-2}$ , and then switches to decrease linearly back to 0 V in 5 ms. The cycle then repeats. (You might want to make a good sketch of the voltage waveform.)

Make a good *quantitative* sketch of the capacitor current as a function of time.