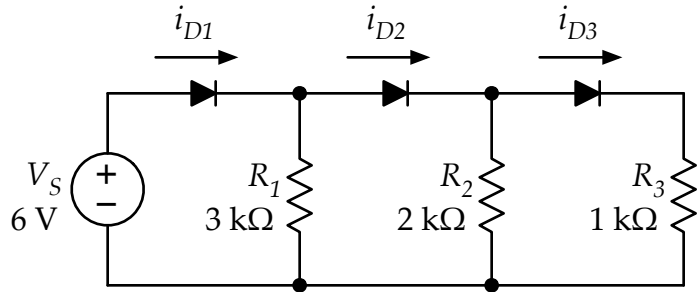


Find the current flowing in each of the diodes in the circuit at right. Use the on/off model for the diodes



$i_{D1} =$ _____ $i_{D2} =$ _____ $i_{D3} =$ _____

Repeat for $V_S = 1.5\text{ V}$.

$i_{D1} =$ _____ $i_{D2} =$ _____ $i_{D3} =$ _____