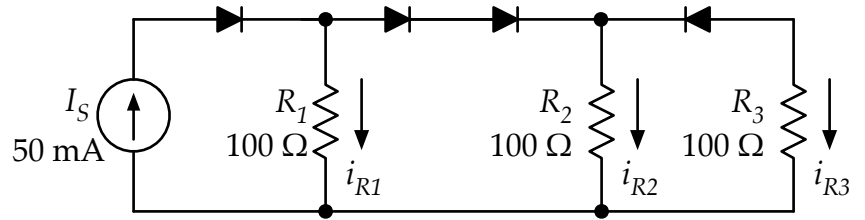


Find the current flowing in each of the resistors in the circuit at right. Use the on/off model for the diodes.



$i_{R1} =$  \_\_\_\_\_  $i_{R2} =$  \_\_\_\_\_  $i_{R3} =$  \_\_\_\_\_