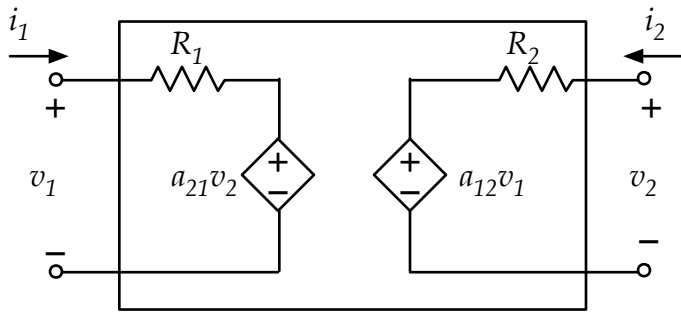
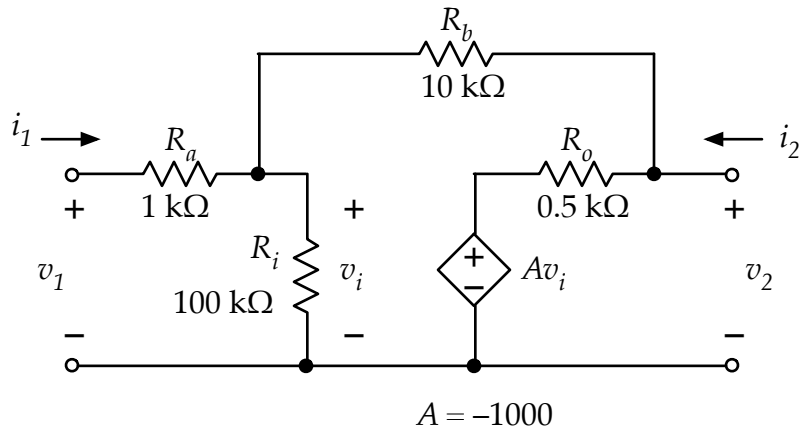


Determine the two-port equivalent for the circuit shown



$R_1 =$ _____ $a_{21} =$ _____

$R_2 =$ _____ $a_{12} =$ _____