

For the circuit shown, determine the Thevenin equivalent at the port defined by the nodes a and b . Sketch the Thevenin equivalent circuit below — be sure to give the values of V_{Th} and R_{Th} for the circuit.

What is the maximum power that this circuit will be able to deliver to a load attached to the port.

P_L (max) = _____

