

The potentiometer in the circuit is adjusted until the power dissipated in it is 1.5 W. Find the value of  $R_P$  that satisfies this condition.

$R_P =$  \_\_\_\_\_

