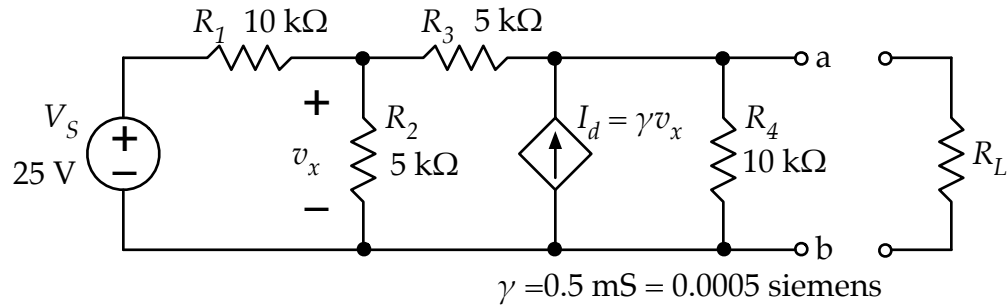


For the circuit shown below, a load resistor will be attached at the port defined by the nodes a and b . What value of R_L will give the maximum power dissipation in the load? If R_L has that value, what is the power that will be dissipated in the load?



$R_L =$ _____ $P_L (\text{max}) =$ _____