

For the circuit below, find the parameters for the Thevenin and Norton equivalent circuits.

$V_{Th} =$  \_\_\_\_\_

$I_N =$  \_\_\_\_\_

$R_{Th} =$  \_\_\_\_\_

