

Find the Thevenin and Norton equivalents with respect to terminals *a* and *b* for the circuit shown below.

$V_{Th} =$ _____

$R_{Th} =$ _____

$I_N =$ _____

