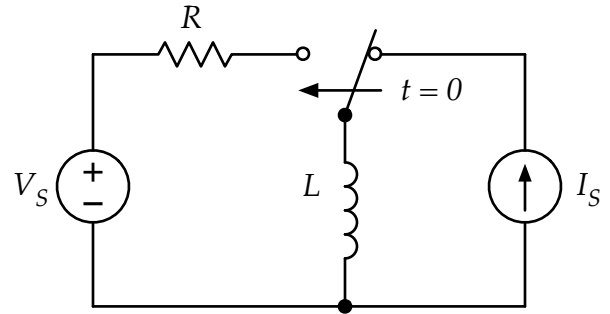


In the circuit shown, the switch flips from the right to the left at $t = 0$. the expressions for the inductor current and voltage for $t > 0$ are:



$$i_L(t) = 4 \text{ A} + (4 \text{ A}) \cdot e^{-t/0.025 \text{ s}}$$

$$v_L(t) = (-80\text{V}) \cdot e^{-t/0.025 \text{ s}}$$

a) Specify the numerical values for V_S , I_S , R and L .

b) At what time during the transient does the energy stored in the inductor reach 9 J?

$V_S =$ _____ ; $I_S =$ _____

$R =$ _____ ; $L =$ _____

$t(E = 9 \text{ J}) =$ _____