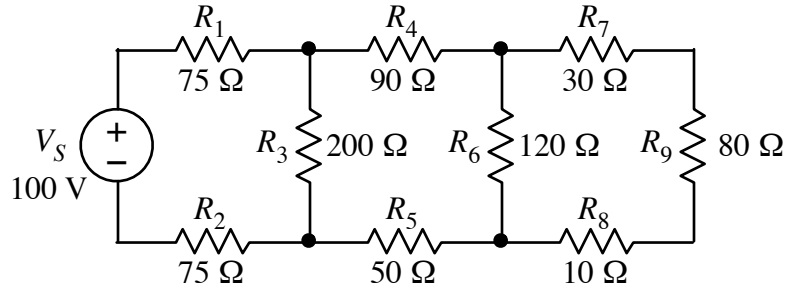


**Problem 1**


- a. For the circuit at right, determine the power delivered by the source.

$P_{V_S} =$  \_\_\_\_\_




- b. For the circuit at right, determine the power delivered by the source.

$P_{I_S} =$  \_\_\_\_\_

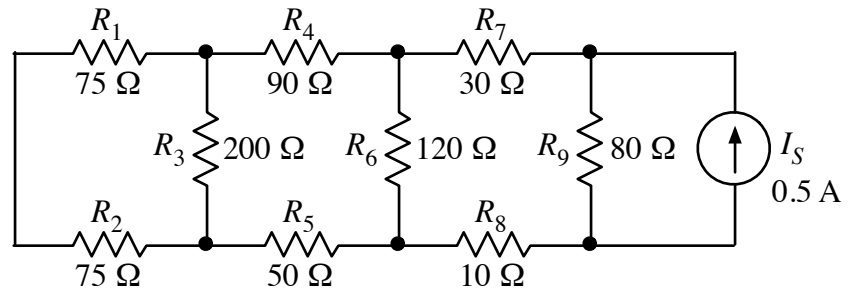
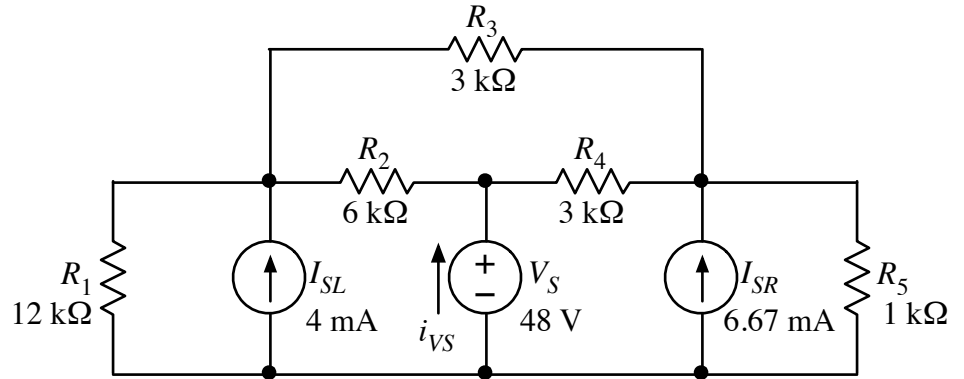
## Problem 2

For the circuit, find the current flowing in the voltage source.




$$i_{VS} = \underline{\hspace{10em}}$$

**Problem 3**


In the circuit at right, find the current  $i_{R2}$ .

$i_{R2} =$  \_\_\_\_\_

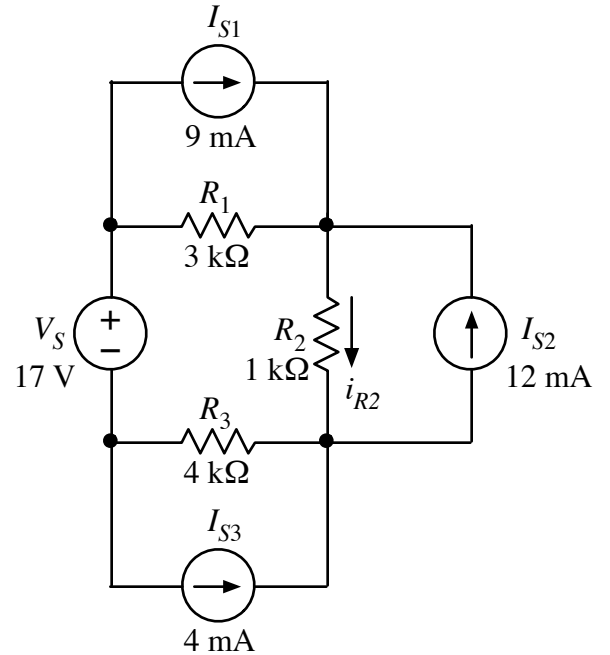

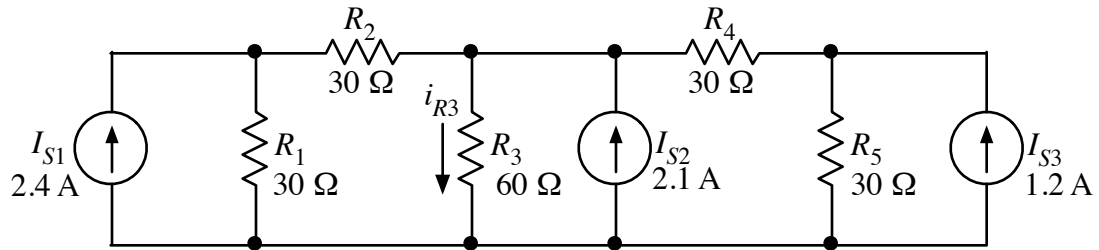**Problem 4**

In the circuit below, find the current  $i_{R3}$ .



$i_{R3} =$  \_\_\_\_\_

<p><b>General info:</b></p> $i = \frac{dQ}{dt} \quad V = \frac{E}{Q}$ <p>Charge on an electron: <math>1.6 \times 10^{-19}</math> C</p> <p>Ohm's law: <math>v_R = i_R R</math></p> <p>power</p> $P_R = \frac{dE}{dt} = v \cdot i$ <p>power dissipated in a resistor</p> $P_R = i_R^2 R = \frac{v_R^2}{R}$ <p>1 kW-hr = <math>3.6 \times 10^6</math> joules</p> <p><b>Resistor combinations:</b></p> <p>Series</p> $R_S = R_1 + R_2 + R_3 \dots$ <p>Parallel</p> $R_P^{-1} = R_1^{-1} + R_2^{-1} + R_3^{-1} \dots$ <p><b>Dividers:</b></p> <p>Voltage divider</p> $v_n = \left[ \frac{R_n}{R_1 + R_2 + R_3 \dots} \right] V_S$ <p>Current divider</p> $i_n = \left[ \frac{R_n^{-1}}{R_1^{-1} + R_2^{-1} + R_3^{-1} \dots} \right] I_S$	<p><b>Node voltage:</b></p> <ol style="list-style-type: none"> <li>1. Identify nodes.</li> <li>2. Choose ground.</li> <li>3. Note any nodes with known voltages (due to voltage sources).</li> <li>4. Identify resistor currents with directions.</li> <li>5. Use KCL to relate currents at each node.</li> <li>6. Use Ohm's law to relate resistor current to node voltages.</li> <li>7. Solve node voltage equations.</li> </ol> <p><b>Mesh current:</b></p> <ol style="list-style-type: none"> <li>1. Identify meshes.</li> <li>2. Note any meshes with known currents (due to current sources).</li> <li>3. Identify resistor voltages, with polarities.</li> <li>4. Use KVL to relate voltages around each mesh.</li> <li>5. Use Ohm's law to relate resistor voltages to node voltages. (Be careful with directions!)</li> <li>6. Solve mesh current equations.</li> </ol> <p><b>Superposition:</b></p> <ol style="list-style-type: none"> <li>1. De-activate all sources except one. (Short voltage sources; open current sources.)</li> <li>2. Solve for desired voltages and currents using reductions, dividers, and transformations to obtain partial results. (Can use node-voltage &amp; mesh-current, too.)</li> <li>3. Repeat for each independent source.</li> <li>4. Add all partial results to obtain total result for each voltage and current.</li> </ol>
--	---

## Source transformations

